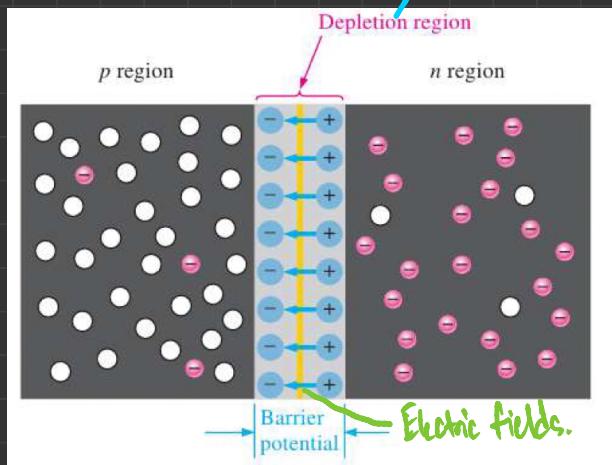


## ① [ The PN Junction ].



N-type.

- major: free  $e^-$
- minor: hole

P-type.

- major: hole
- minor: free  $e^-$


- n region losing free electrons, as they drifts across the junction
  - p region losing hole as the free  $e^-$  and holes combine.

Note! ອັນດຸກໂຕຣະເນົມກ່ອນລົມ.

- ໃນໄຊຮະໂລດອນ  $e^-$  ມີເພື່ອ Depletion region. ແຕ່ລົງທຶນພົມພາກຕະຫຼາດ  
ມາຊີ້ວຍໜີ້ແກ່ໃນ  $e^-$  ມີເພື່ອລົບສະບາຍຸມາໃຫຍ່ໄປຢູ່.

The typical Barrier Potential is 0.7 V (for silicon)  
0.3 V (for germanium)  $\rightarrow 25^{\circ}\text{C}$


## ② [Diode Operation].

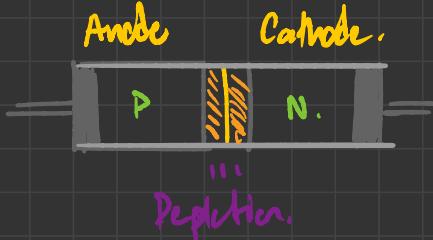

Semiconductor (Silicon  $\approx 0.8 \text{ V}$ )

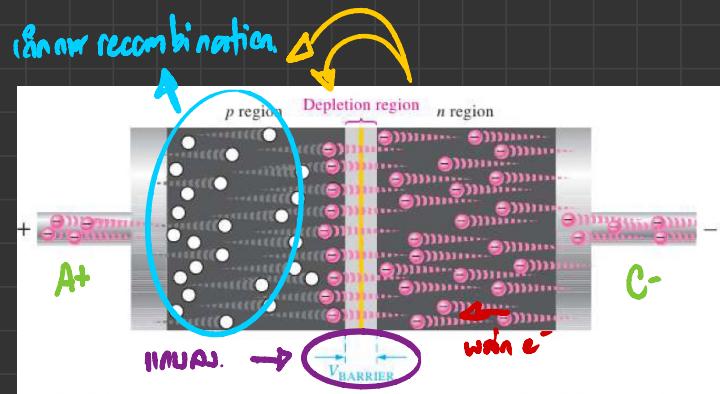
## [2.1] Forward Bias. (ໄຟຈົກງານ)

↳ the condition that permits current through a pn junction.



Note!  $V_{\text{bias min}} > 0.7 \text{ V.}$  (ສະໜັບ)

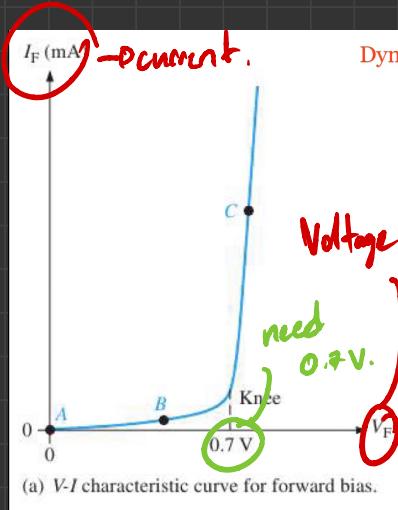V-I Characteristic for (Forward Bias) → graph expt.



**Exponential Diode**  
The exponential diode model represents the following relationship between the diode current  $I$  and the diode voltage  $V$ :

$$I = IS \cdot \left( e^{\frac{qV}{NkT_m}} - 1 \right) \quad V > -BV$$

$$I = -IS \cdot \left( e^{\frac{-q(V+1)}{NkT_m}} - e^{\frac{-qV}{NkT_m}} \right) \quad V \leq -BV$$

where:

- $q$  is the elementary charge on an electron ( $1.602176 \times 10^{-19}$  coulombs).
- $k$  is the Boltzmann constant ( $1.3806503 \times 10^{-23}$  J/K).
- $BV$  is the Reverse breakdown voltage parameter value.
- $N$  is the emission coefficient.
- $IS$  is the saturation current.
- $T_m$  is the temperature at which the diode parameters are specified, as defined by the Measurement temperature parameter value.

When  $(qV/NkT_m) > 80$ , the block replaces  $e^{\frac{qV}{NkT_m}}$  with  $(qV/NkT_m - 79)e^{80}$ , which matches the gradient of the diode current at  $(qV/NkT_m) = 80$  and extrapolates linearly. When  $(qV/NkT_m) < -79$ , the block replaces  $e^{\frac{-qV}{NkT_m}}$  with  $(qV/NkT_m + 79)e^{-80}$ , which also matches the gradient and extrapolates linearly. Typical electrical circuits do not reach these extreme values. The block provides this linear extrapolation to help convergence when solving for the constraints during simulation.

↳ ລັບສິມຸලັກ ມາຍ.


Note!  
Symbol.  
 Cathode.  
Anode

- $V_{\text{bias}} > 0.7 \text{ V}$  (ສີ) $I_W$
- Semiconductor ອົງກອນ  
 ນຳໃຫຍ່ໄຟຈົກງານ.

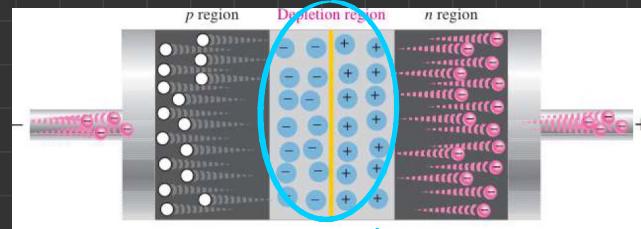
## [2.2] Reverse Bias (ឈុត្រការណ៍ស្តី)

↳ the condition that prevents current through the pn junction.


Note! \* Reverse current can be produced by minority carriers  $\downarrow$ .  
 (small current)




ស្រាវជ្រាវ. (រៀងគេលូន)

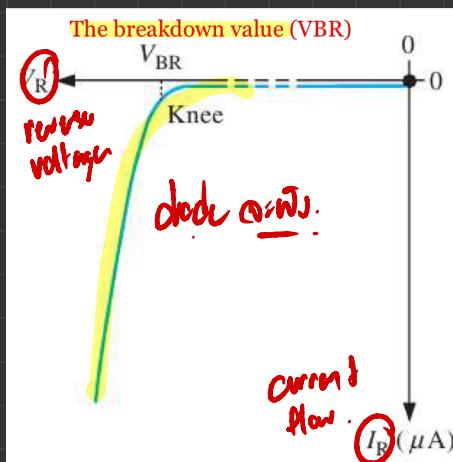


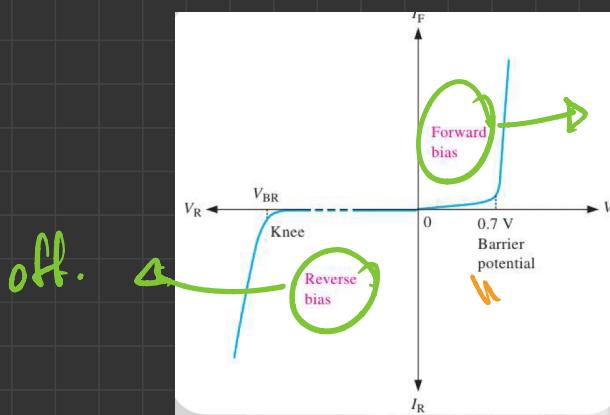
- មិនអាចបញ្ចប់ទូទាត់បាន.
- ការបូនគិត.
- typical rectifier diode
- a breakdown voltage around  $V_B > 50V$ . Some are  $5V_B$ .




## [2.3]. Ideals and Application.

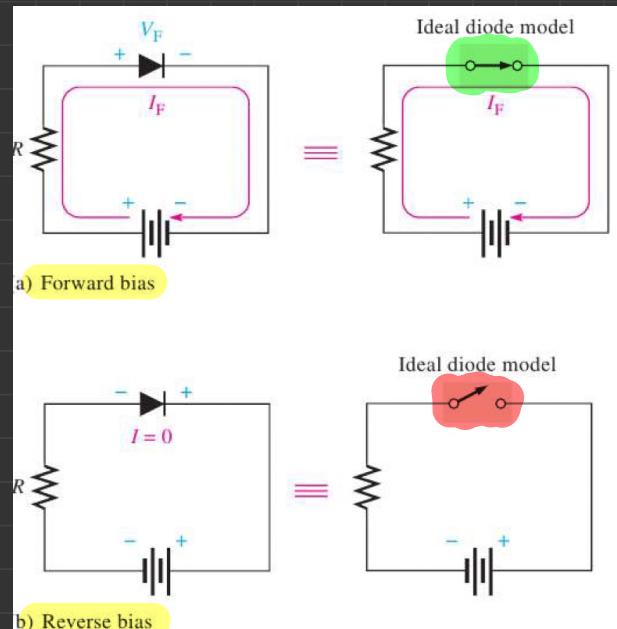

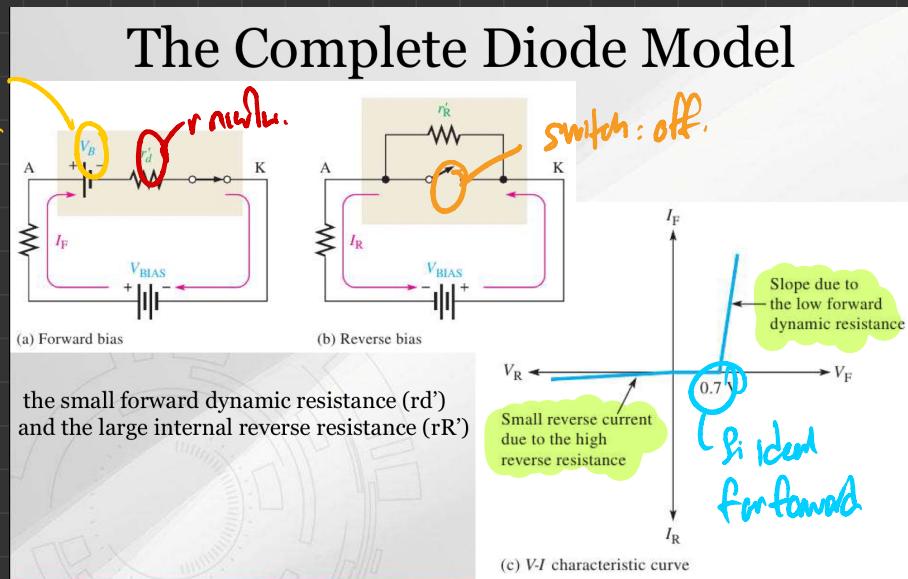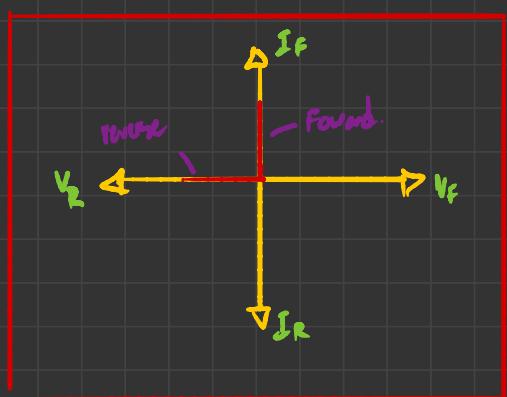- Diode  $\rightarrow$  switch with low resistance.
- ຖិន្នន័យ  
forward bias,  $\rightarrow$  switch : ON.  
reverse bias,  $\rightarrow$  switch : OFF.



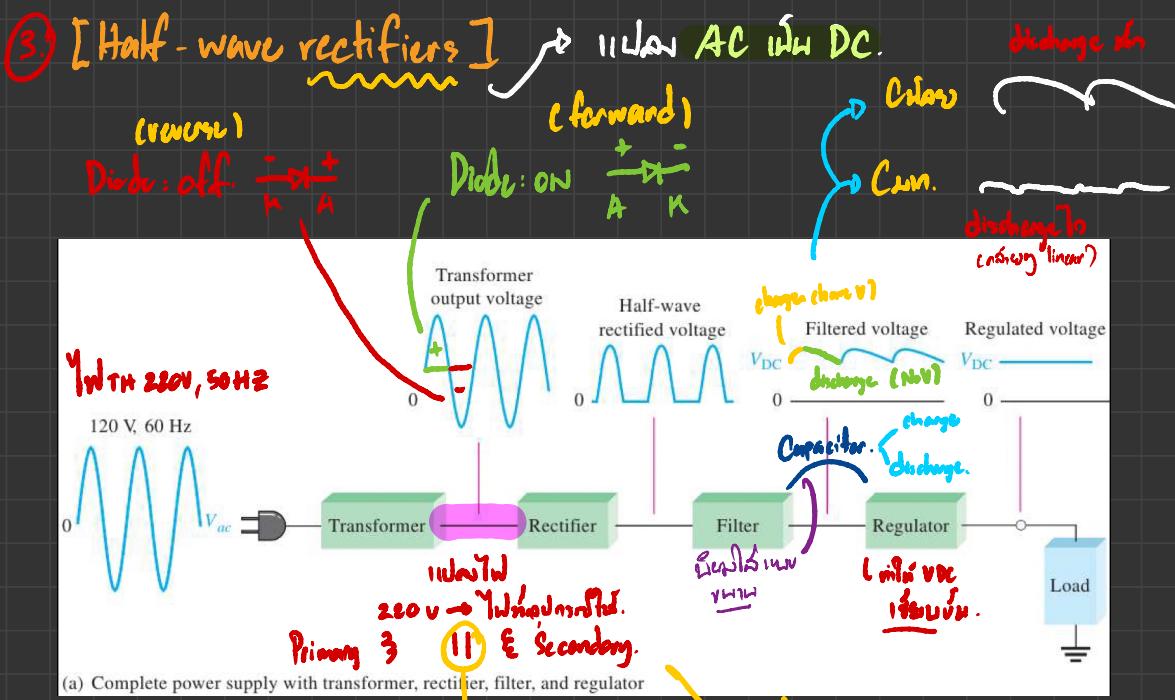

(a) Complete power supply with transformer, rectifier, filter, and regulator


Turns Ratio.

volt

$$\frac{N_p}{N_s} = \frac{V_p}{V_s} = n$$

coats.


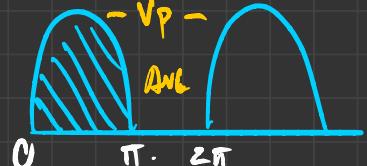
$\left\{ \begin{array}{l} \text{if } V_p > V_s \text{ (step up)} \\ \text{if } V_p < V_s \text{ (step down)} \end{array} \right.$



### [3.1] Half-wave cat.

Diode: ON.  
(forward)

pract.

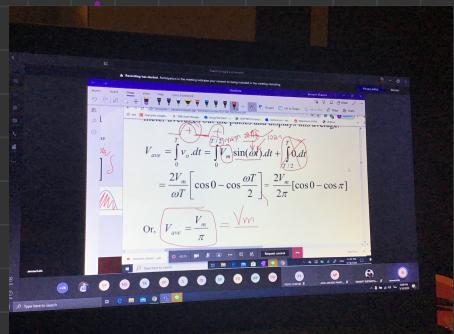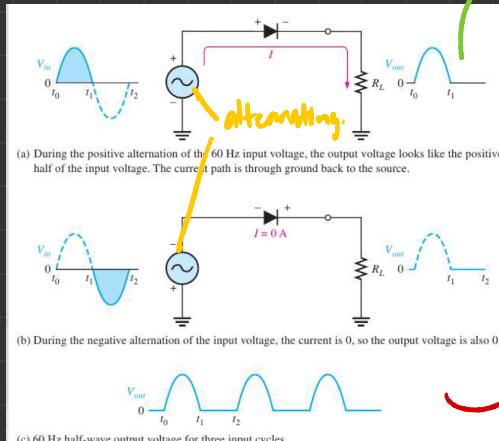


(reverse)


Diode: off.

$$V_{AVG.} = V_p / \pi.$$

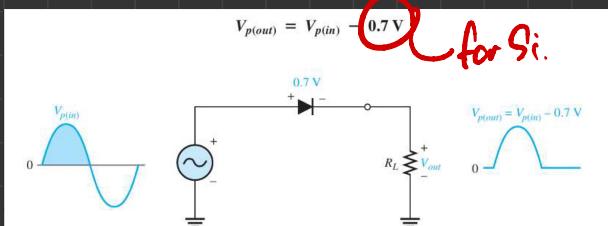
# Effect of Barrier Potential. (specific rectifier)



Peak Inverse Voltage.

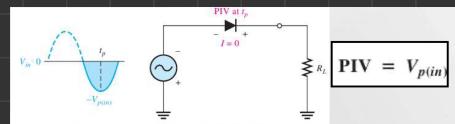

## ④ [Full-wave rectifiers].

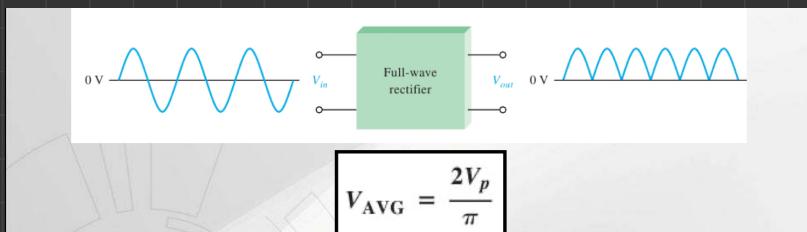




• Double of half wave.  
Ex:  $31.1 \text{ V} \rightarrow 63.6 \text{ V}$ .

### [4.1] Center-tapped full wave.

○ unswivin Vin -  $\rightarrow$  Vout -  
dot. Vin +  $\rightarrow$  Vout +

Note! gain effect ratio.

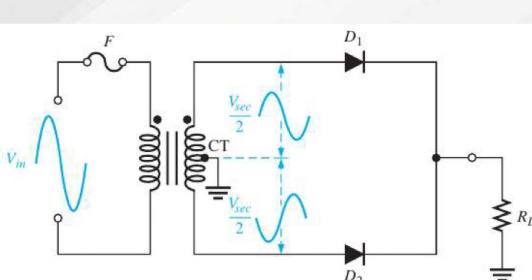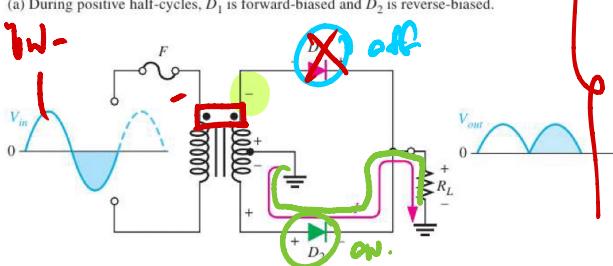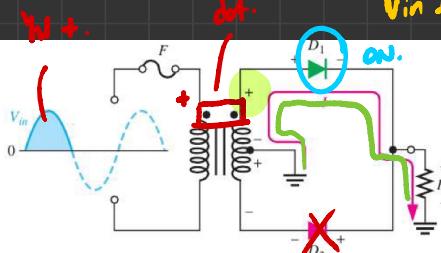ratio 1  $\rightarrow \frac{V_{pcpi}}{2} - 0.7 \text{ V}$ .




A center-tapped full-wave rectifier.


fusion. = full wave.

ratio 2  $\rightarrow \left( \frac{V_{pcpi}}{2} \times 2 \right) - 0.7 \text{ V}$

## ⑤ [full bridge Operation]

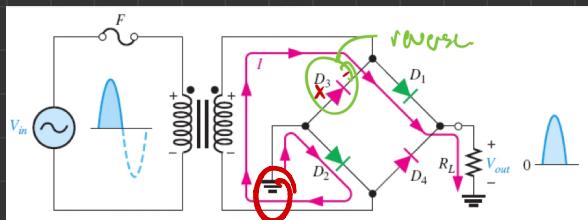

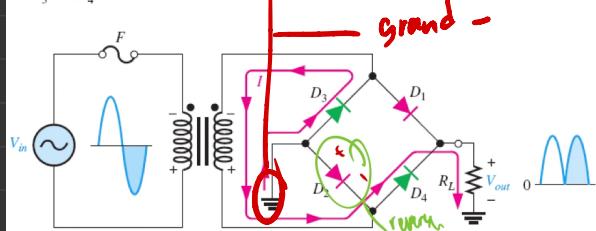
(a) During the positive half-cycle of the input,  $D_1$  and  $D_2$  are forward-biased and conduct current.  $D_3$  and  $D_4$  are reverse-biased.



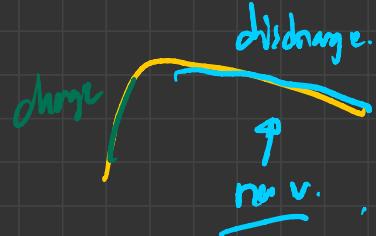
(b) During the negative half-cycle of the input,  $D_3$  and  $D_4$  are forward-biased and conduct current.  $D_1$  and  $D_2$  are reverse-biased.

$$2 \text{ diodes} = 0.7 \times 2 \rightarrow$$

$$V_{peak} = V_{p(sec)} - 1.4 \text{ V.}$$





## Peak Inverse Voltage.

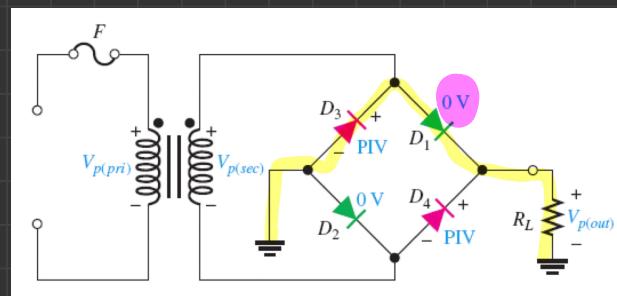

(a) For the ideal diode model (forward-biased diodes  $D_1$  and  $D_2$  are shown in green),  $\text{PIV} = V_{p(out)}$ .

## [5.2] Ripples Filters

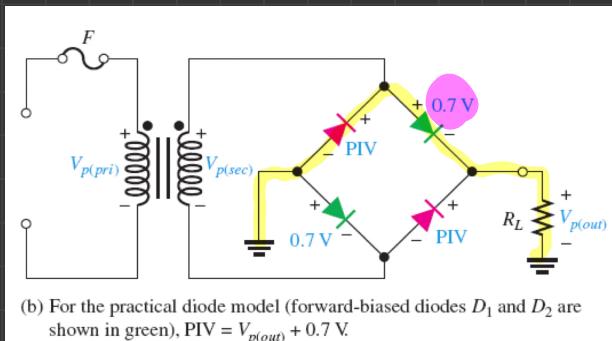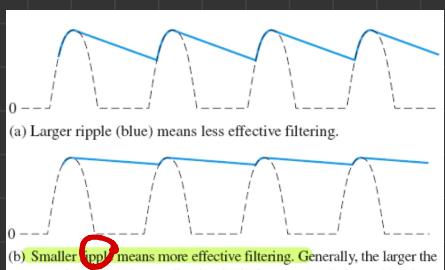(D) Continuous Capacitor  
Resistance =  $R \cdot C$



(b) For the practical diode model (forward-biased diodes  $D_1$  and  $D_2$  are shown in green),  $\text{PIV} = V_{p(out)} + 0.7 \text{ V.}$

$$r = V_{ripple} / V_{dc}$$


$R, L, C$  Increase

then  $V_r$  decrease

and  $V_{DC}$  increase.


# ⑥ Regulated Power supply.

## Regulated power supply

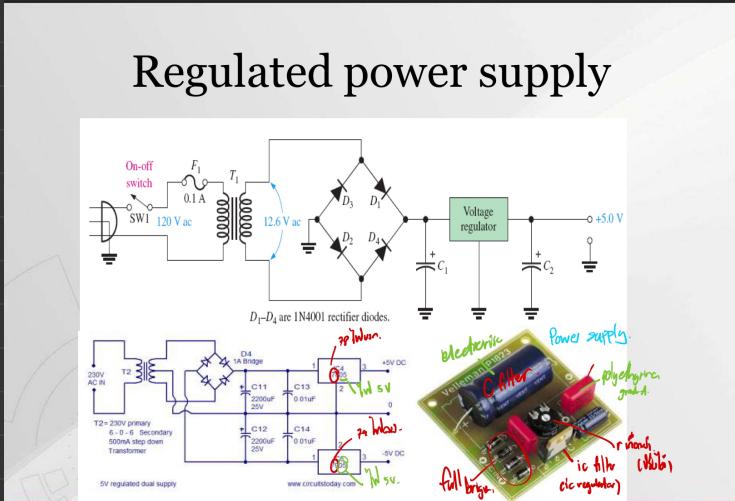


## ⑦ Clippers and Limiters


### Diode Limiters or clipper

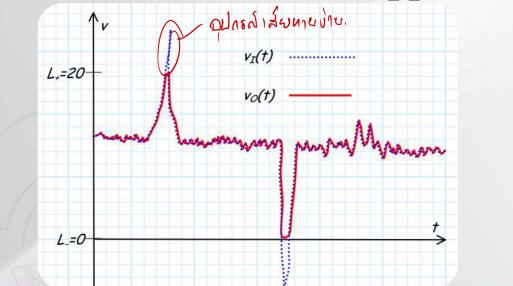

### Diode Limiters or clipper

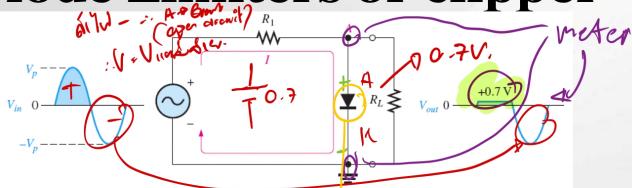

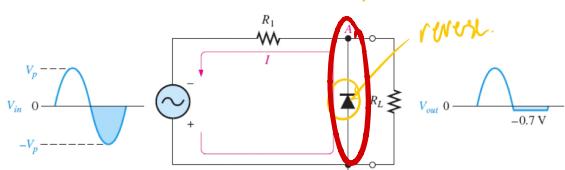(a) Limiting of the positive alternation. The diode is forward-biased during the positive alternation (above 0.7 V) and reverse-biased during the negative alternation.



(b) Limiting of the negative alternation. The diode is forward-biased during the negative alternation (below -0.7 V) and reverse-biased during the positive alternation.