

Final:
~~~~~

Op-Amp.  
Semiconductor physios.  
Diode.

Diode Application.  
transistor.  
transistor Application.


# Alexander-Sadiku

## Fundamentals of Electric Circuits

### Chapter 5

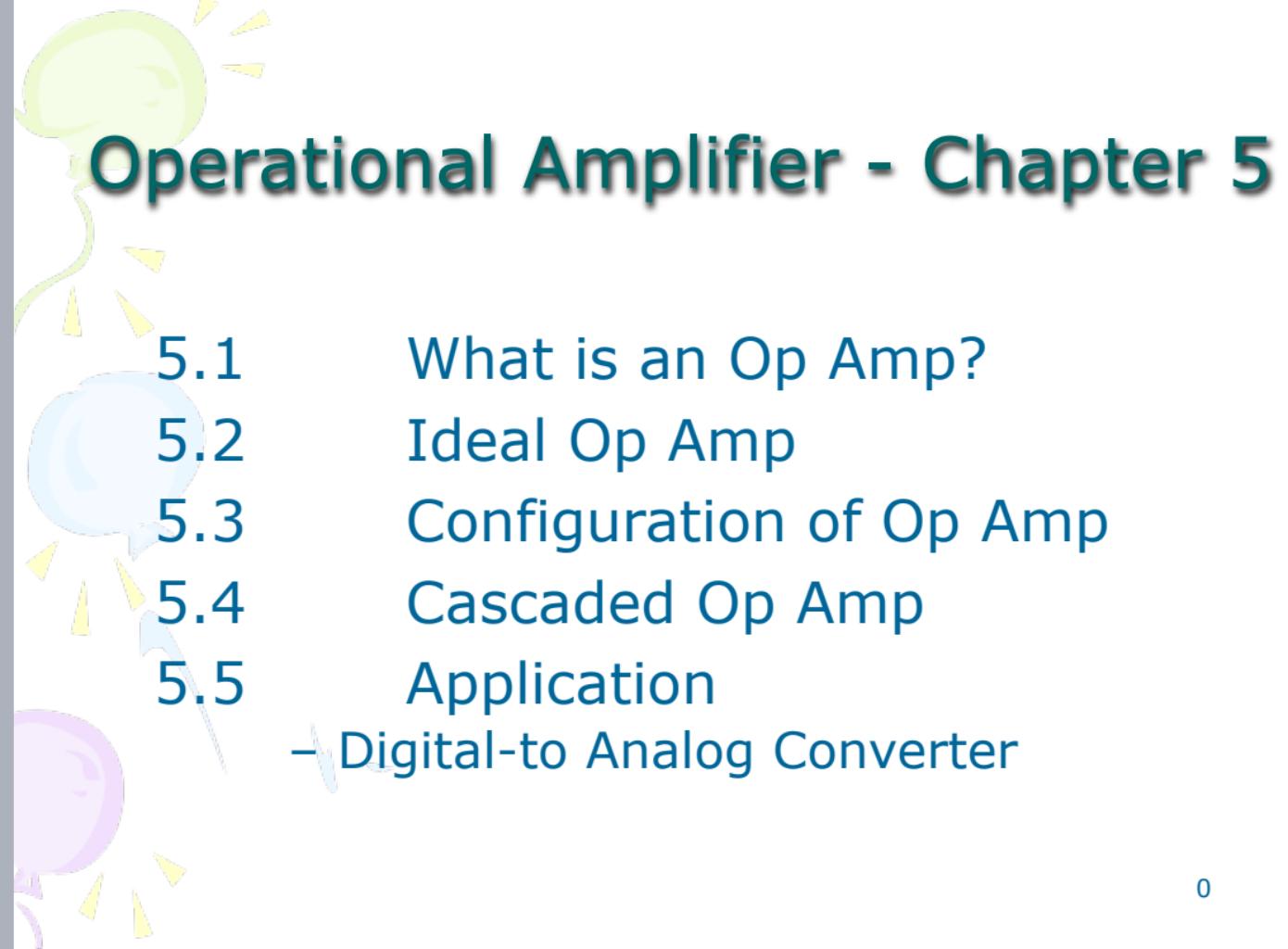
#### Operational Amplifier

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



# Operational Amplifier - Chapter 5

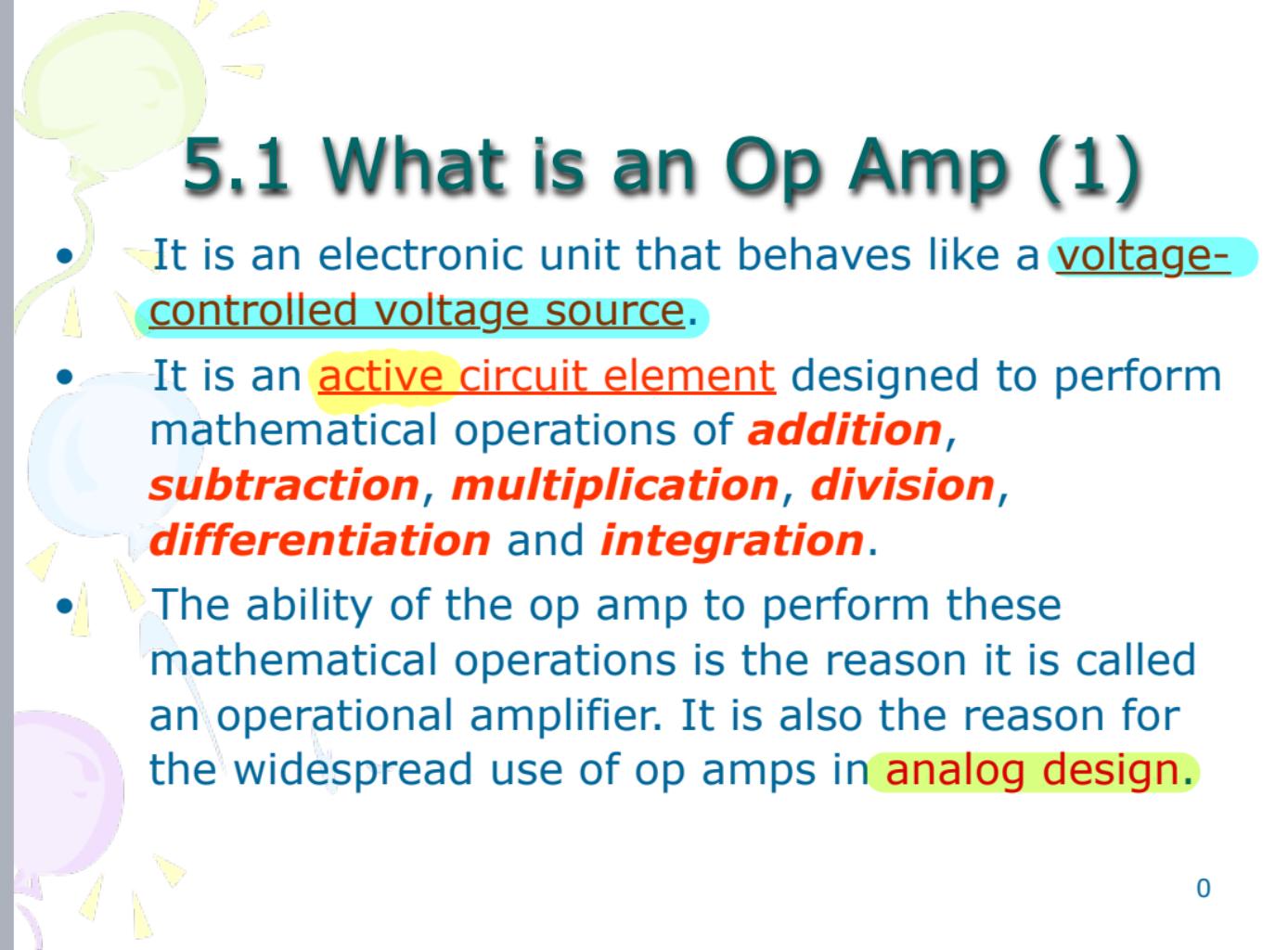- 5.1      What is an Op Amp?
- 5.2      Ideal Op Amp
- 5.3      Configuration of Op Amp
- 5.4      Cascaded Op Amp
- 5.5      Application
  - Digital-to Analog Converter




## 5.1 What is an Op Amp (1)

- It is an electronic unit that behaves like a voltage-controlled voltage source.
- It is an active circuit element designed to perform mathematical operations of **addition, subtraction, multiplication, division, differentiation** and **integration**.
- The ability of the op amp to perform these mathematical operations is the reason it is called an operational amplifier. It is also the reason for the widespread use of op amps in analog design.

# 5.1 What is an Op Amp (2)

|                    |   |   |               |
|--------------------|---|---|---------------|
| Balance            | 1 | 8 | No connection |
| Inverting input    | 2 | 7 | $V^+$         |
| Noninverting input | 3 | 6 | Output        |
| $V^-$              | 4 | 5 | Balance       |

(a)

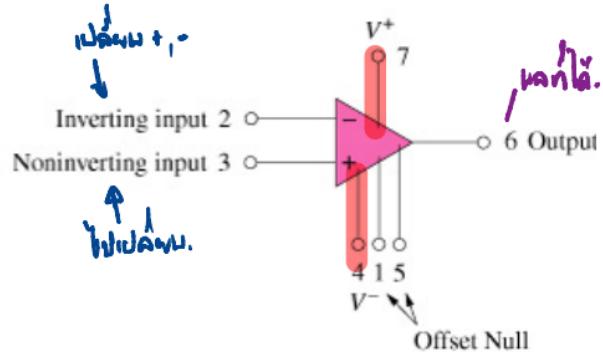


(b)


A typical op amp: (a) pin configuration, (b) circuit symbol
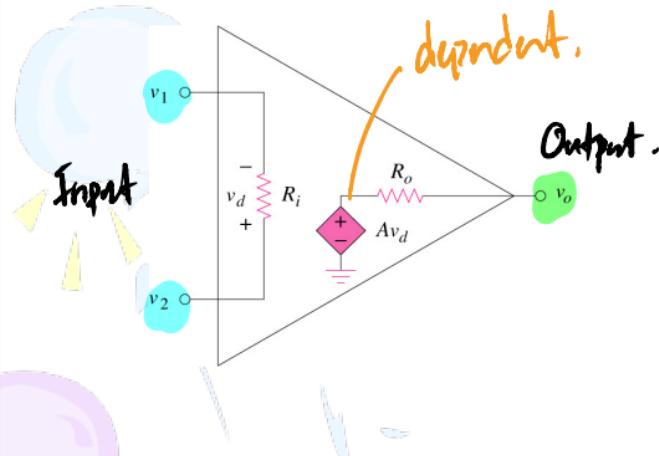
# 5.1 What is an Op Amp (3)

The equivalent circuit  
Of the non-ideal op amp



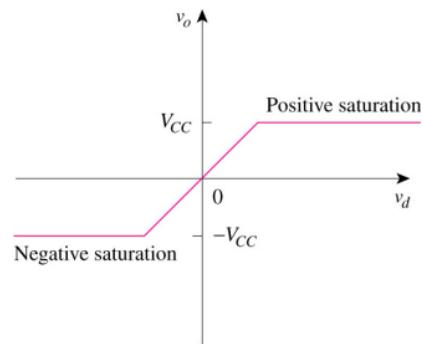Op Amp output:  
 $v_o$  as a function of  $V_d$



$$v_d = v_2 - v_1; \quad v_o = Avd = A(v_2 - v_1)$$

# 5.1 What is an Op Amp (4)

Typical ranges for op amp parameters

| Parameter                | Typical range                | Ideal values      |
|--------------------------|------------------------------|-------------------|
| Open-loop gain, A        | $10^5$ to $10^9$ $\Omega$    | $\infty$ $\Omega$ |
| Input resistance, $R_i$  | $10^6$ to $10^{10}$ $\Omega$ | $\infty$ $\Omega$ |
| Output resistance, $R_o$ | 10 to 100 $\Omega$           | 0 $\Omega$        |
| Supply voltage, $V_{CC}$ | 5 to 24 V                    |                   |

## 5.2 Ideal Op Amp (1)

An ideal op amp has the following characteristics:


① No current flow in inputs.

1. Infinite open-loop gain,  $A \approx \infty$
2. Infinite input resistance,  $R_i \approx \infty$
3. Zero output resistance,  $R_o \approx 0$

$$i_1 = 0, \quad i_2 = 0$$

$$v_d = v_2 - v_1 = 0$$

$$v_1 = v_2$$

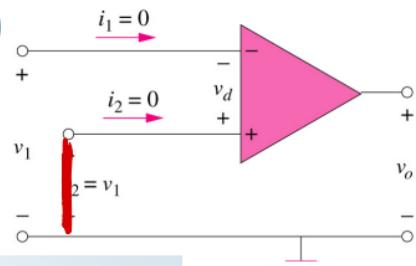

An **ideal op amp** is an amplifier with infinite open-loop gain, infinite input resistance, and zero output resistance.


## 5.2 Ideal Op Amp (2)

Example 1:

Determine the value of  $i_o$ .

$$\frac{V_o - 1}{40} = \frac{1}{5}$$

$$\therefore V_o = 9 \text{ V.}$$

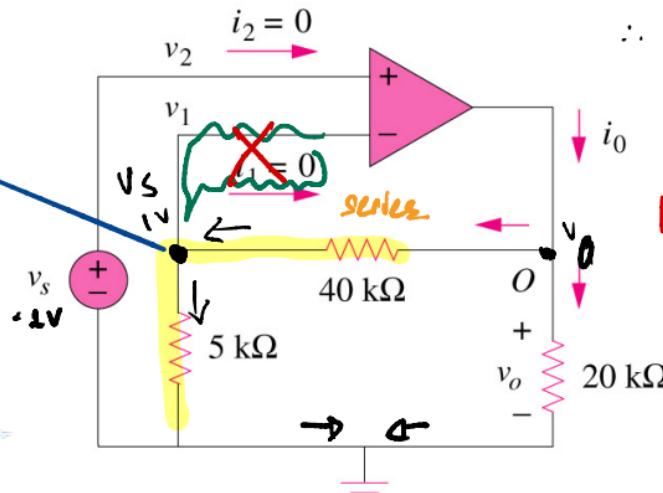

KCL

$$\frac{V_o}{20\text{ k}} + \frac{V_o - 1}{20\text{ k}} = i_o$$

$$\therefore \frac{9}{20\text{ k}} + \frac{8}{20\text{ k}} = i_o$$

$$\therefore i_o = 0.65 \text{ mA.}$$


KCL

\*Refer to in-class illustration, textbook

Ans: 0.65mA
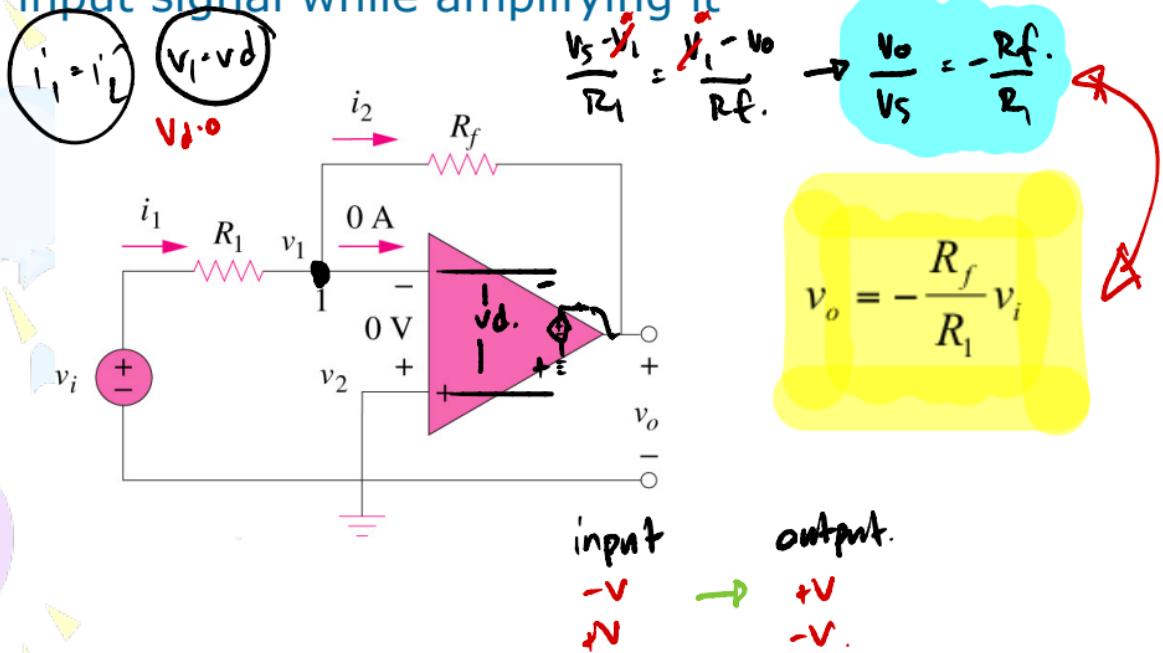
## 5.3 Configuration of Op amp (1)

- Inverting amplifier reverses the polarity of the input signal while amplifying it



## 5.3 Configuration of Op amp (2)

### Example 2

Refer to the op amp below. If  $v_i = 0.5V$ , calculate:  
(a) the output voltage,  $v_o$  and (b) the current in  
the  $10k\Omega$  resistor. *find  $v_o$ , find  $i_1$ .*


$$I_1 = \frac{V}{R} = \frac{0.5}{10 \times 10^3} = \frac{5 \times 10^{-4}}{10^4} = 5 \times 10^{-5}$$

$$= 50 \times 10^{-6}$$

*50 nA.*

$$0.5V$$

$v_i$

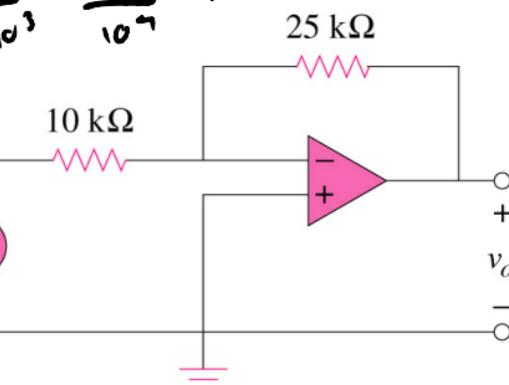

$$v_o = \frac{-25k}{10k} \cdot 0.5$$

$$v_o = -1.25V$$

Ans:


(a) -1.25V; (b) 50μA

\*Refer to in-class illustration, textbook

## 5.3 Configuration of Op amp (3)

- Non-inverting amplifier is designed to produce positive voltage gain

input  $v_i$  +

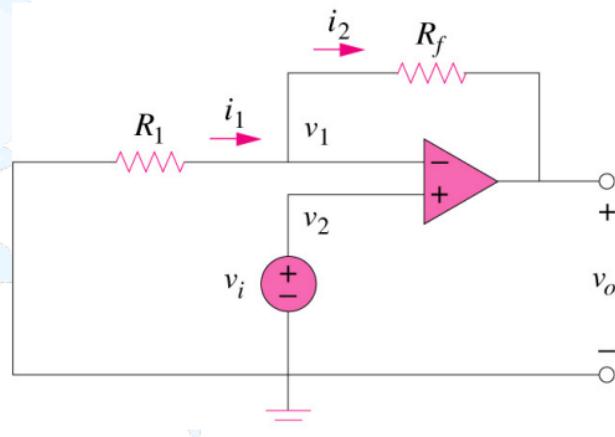


$$v_o = \left(1 + \frac{R_f}{R_1}\right)$$

## 5.3 Configuration of Op amp (4)
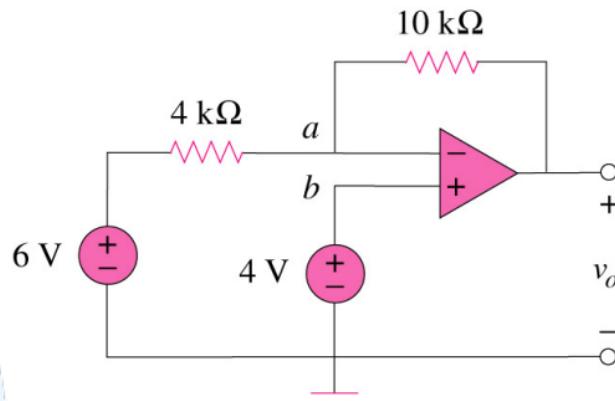
### Example 3

For the op amp shown below, calculate the output voltage  $v_o$ .




\*Refer to in-class illustration, textbook

Ans: -1V

0
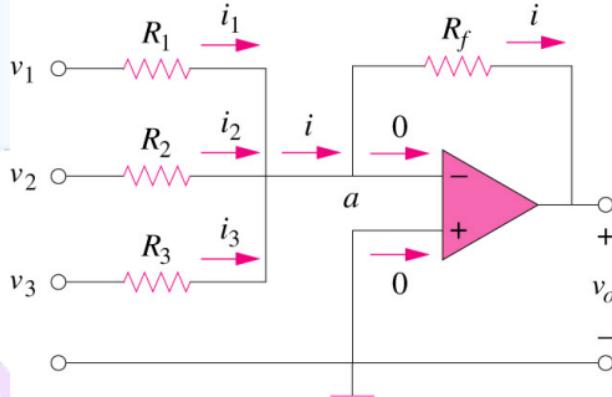
## 5.3 Configuration of Op amp (5)

- Summing Amplifier is an op amp circuit that combines several inputs and produces an output that is the weighted sum of the inputs.




$$v_o = - \left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)$$

## 5.3 Configuration of Op amp (6)
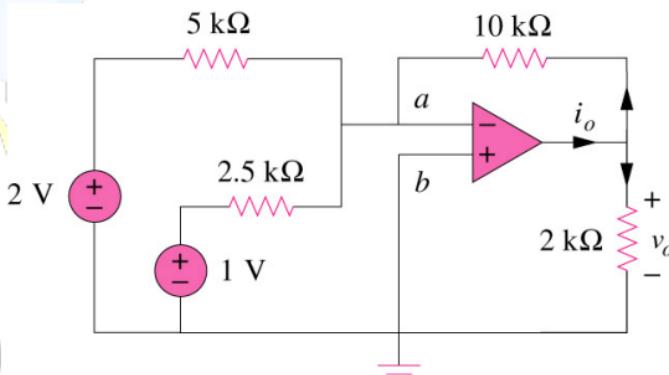
### Example 4

Calculate  $v_o$  and  $i_o$  in the op amp circuit shown below.




\*Refer to in-class illustration, textbook

Ans: -8V, -4.8mA
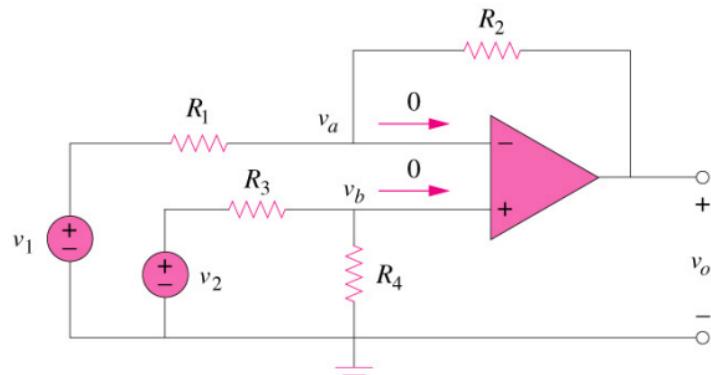
## 5.3 Configuration of Op amp (7)


- Difference amplifier is a device that amplifies the difference between two inputs but rejects any signals common to the two inputs.



$$v_o = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)} v_2 - \frac{R_2}{R_1} v_1 \Rightarrow v_o = v_2 - v_1, \text{ if } \frac{R_2}{R_1} = \frac{R_3}{R_4} = 1$$
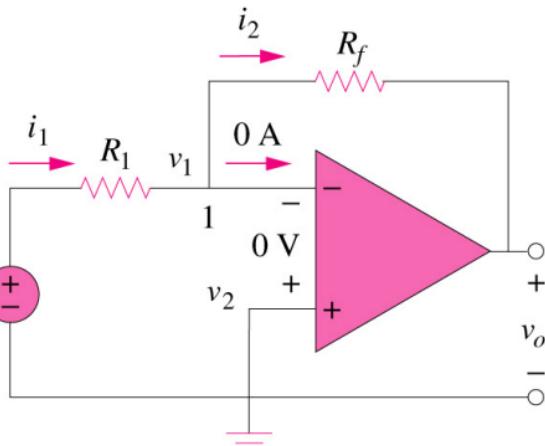
## 5.3 Configuration of Op amp (1)

- Inverting amplifier reverses the polarity of the input signal while amplifying it




$$v_o = -\frac{R_f}{R_1} v_i$$

## 5.3 Configuration of Op amp (6)
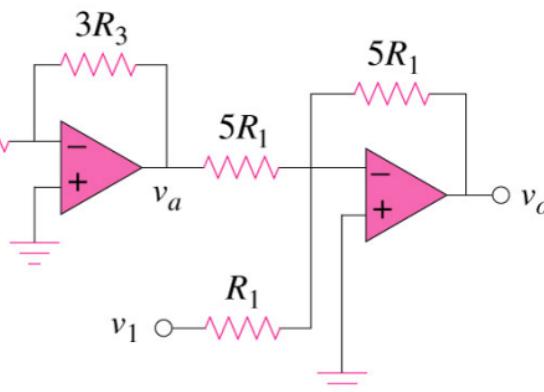
### Example 5

Determine  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  so that  $v_o = -5v_1 + 3v_2$  for the circuit shown below.



Ans:

$$R_1 = 10\text{k}\Omega$$

$$R_2 = 50\text{k}\Omega$$


$$R_3 = 20\text{k}\Omega$$

$$R_4 = 20\text{k}\Omega$$

\*Refer to in-class illustration, textbook
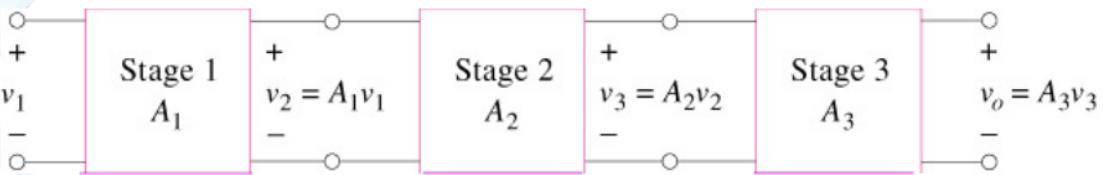
## 5.4 Cascaded Op Amp (1)


- It is a head-to-tail arrangement of two or more op amp circuits such that the output to one is the input of the next.



## 5.4 Cascaded Op Amp (2)
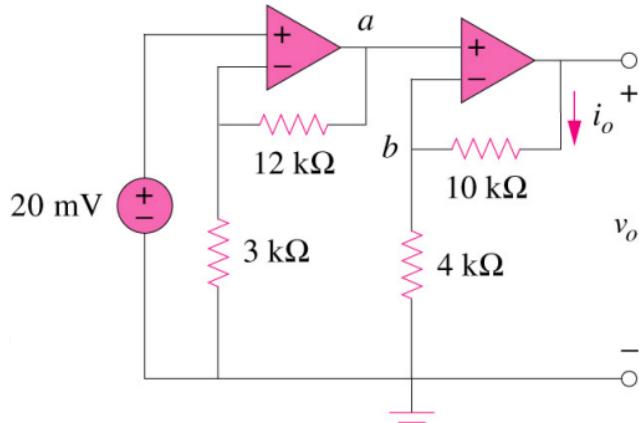
### Example 6

Find  $v_o$  and  $i_o$  in the circuit shown below.




\*Refer to in-class illustration, textbook

Ans:  $350\text{mV}$ ,  $25\mu\text{A}$

## 5.4 Cascaded Op Amp (3)

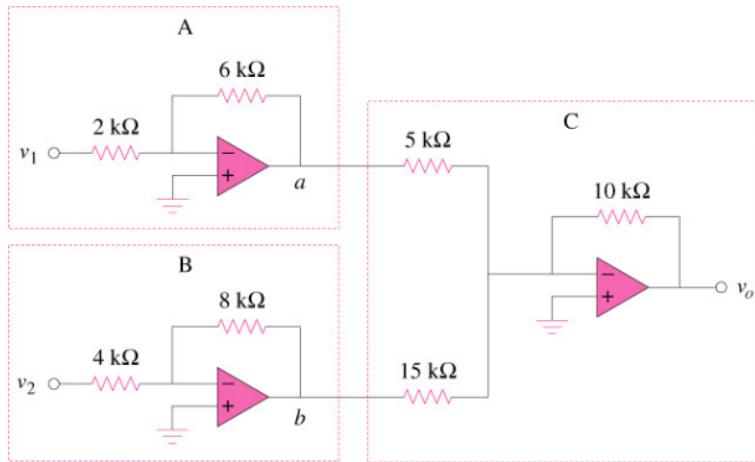Example 7

If  $v_1 = 1V$  and  $v_2 = 2V$ , find  $v_o$  in the op amp circuit shown below.





\*Refer to in-class illustration, textbook

Ans: 8.667 V
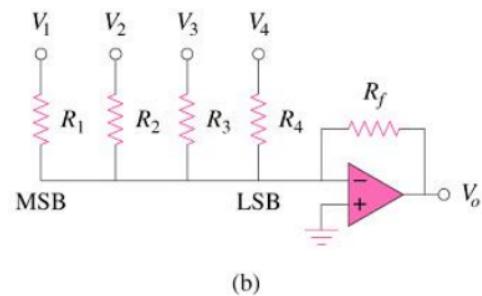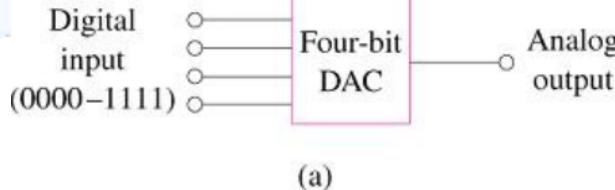
## 5.5 Application (1)

- Digital-to Analog Converter (DAC) : it is a device which transforms digital signals into analog form.

Four-bit DCA: (a) block diagram (b) binary weighted ladder type



$$-V_o = \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 + \frac{R_f}{R_4} V_4$$

where


$V_1$  – MSB,  $V_4$  – LSB

$V_1$  to  $V_4$  are either 0 or 1 V

## 5.5 Application(2)
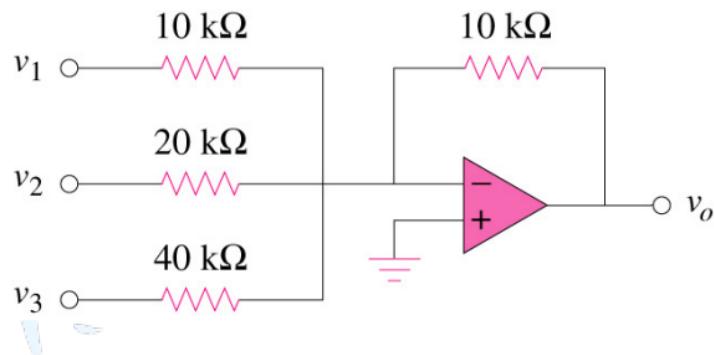
### Example 8

For the circuit shown below, calculate  $v_o$  if  $v_1 = 0V$ ,  $v_2 = 1V$  and  $v_3 = 1V$ .





\*Refer to in-class illustration, textbook


Ans:-0.75V



# Op-amp

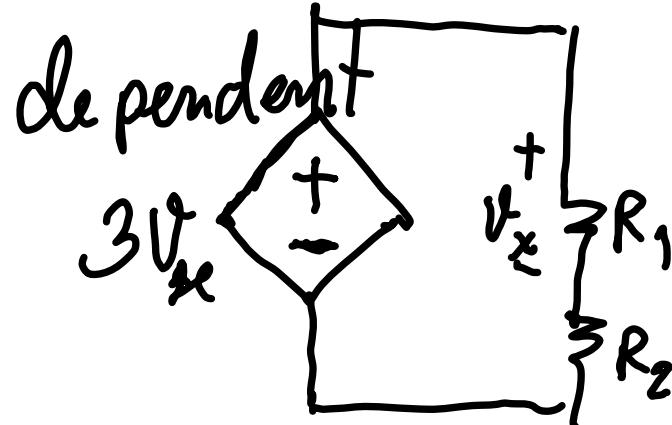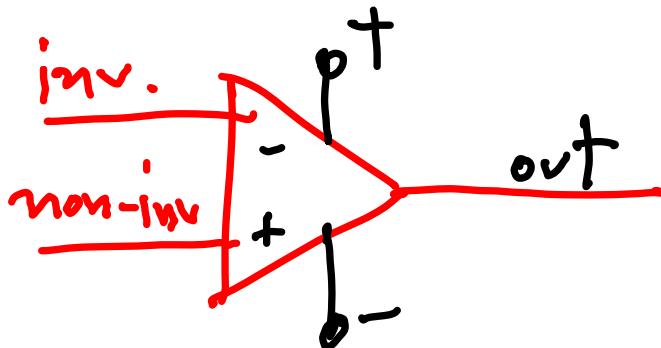

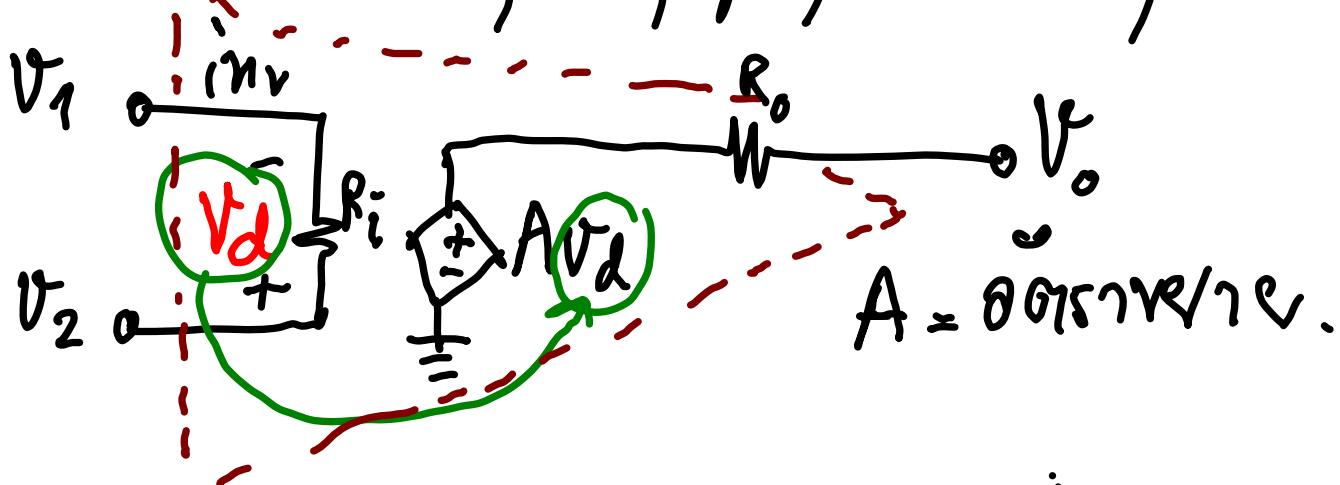- Voltage-controlled voltage source
- ~~ກົດກອບກິລືນຕີ ຂໍມູນມາດີເຄມສອງລະຫວ່າງ~~
- ~~ຊັບຍາຍຈາກຮັບໄດ້ ພາກ, ຄົບ, ອົບ, ດຸນທີ່ສອງ, ດົກກຳ~~





$$V_d = V_2 - V_1 \quad \text{or: } V_o = A V_d = A (V_2 - V_1) \quad \cancel{\times}$$

↙  
↙ A ຖັນຂອງ open-loop voltage gain

| Parameters                                                   | ranges                | Ideal value     |
|--------------------------------------------------------------|-----------------------|-----------------|
| A (Gain) <small>(ວຽກນົກສະເໜີ)</small>                        | $10^5$ ດ້ວຍ $10^8$    | $\infty$        |
| $R_i$ (input Resistance) <small>(input Resistance)</small>   | $10^6$ ດ້ວຍ $10^{13}$ | $\infty \Omega$ |
| $R_o$ (Output Resistance) <small>(Output Resistance)</small> | $10$ ດ້ວຍ $100$       | $0 \Omega$      |

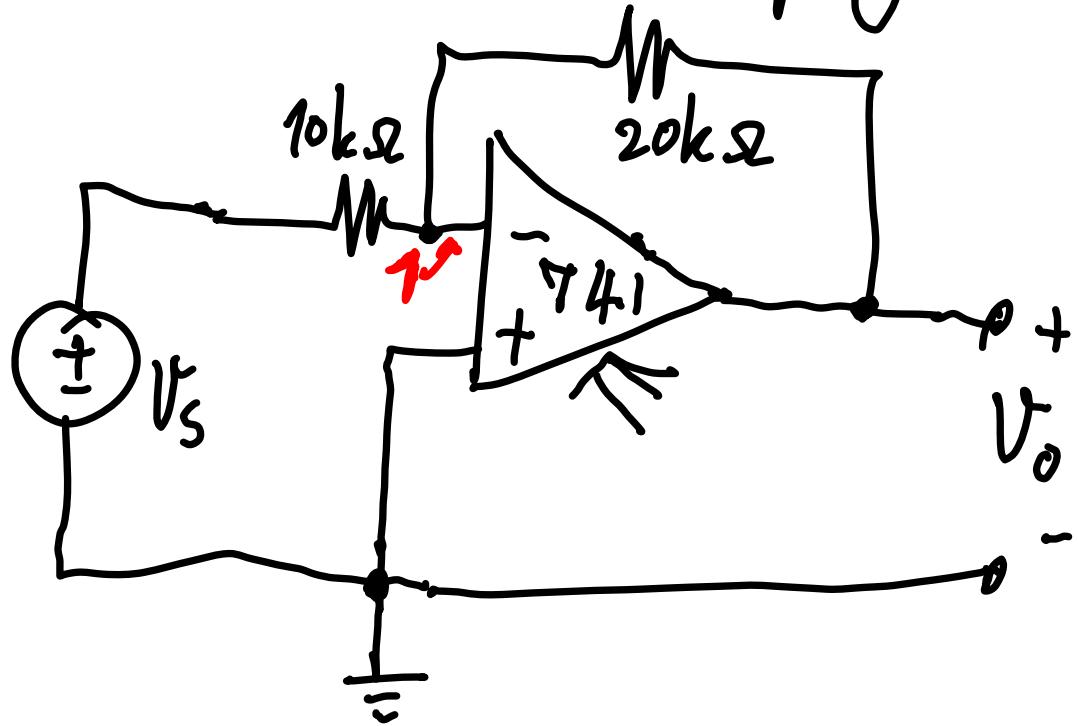Ex Op-Amp 741 ຂອງ open-loop gain ( $A$ )  $2 \times 10^5$   
ມີຄວາມຕ່າງໆ  $2 M\Omega$  ມີຄວາມຕ່າງໆ  $50 \Omega$  ຢັງ close-loop gain  $V_o / V_s$



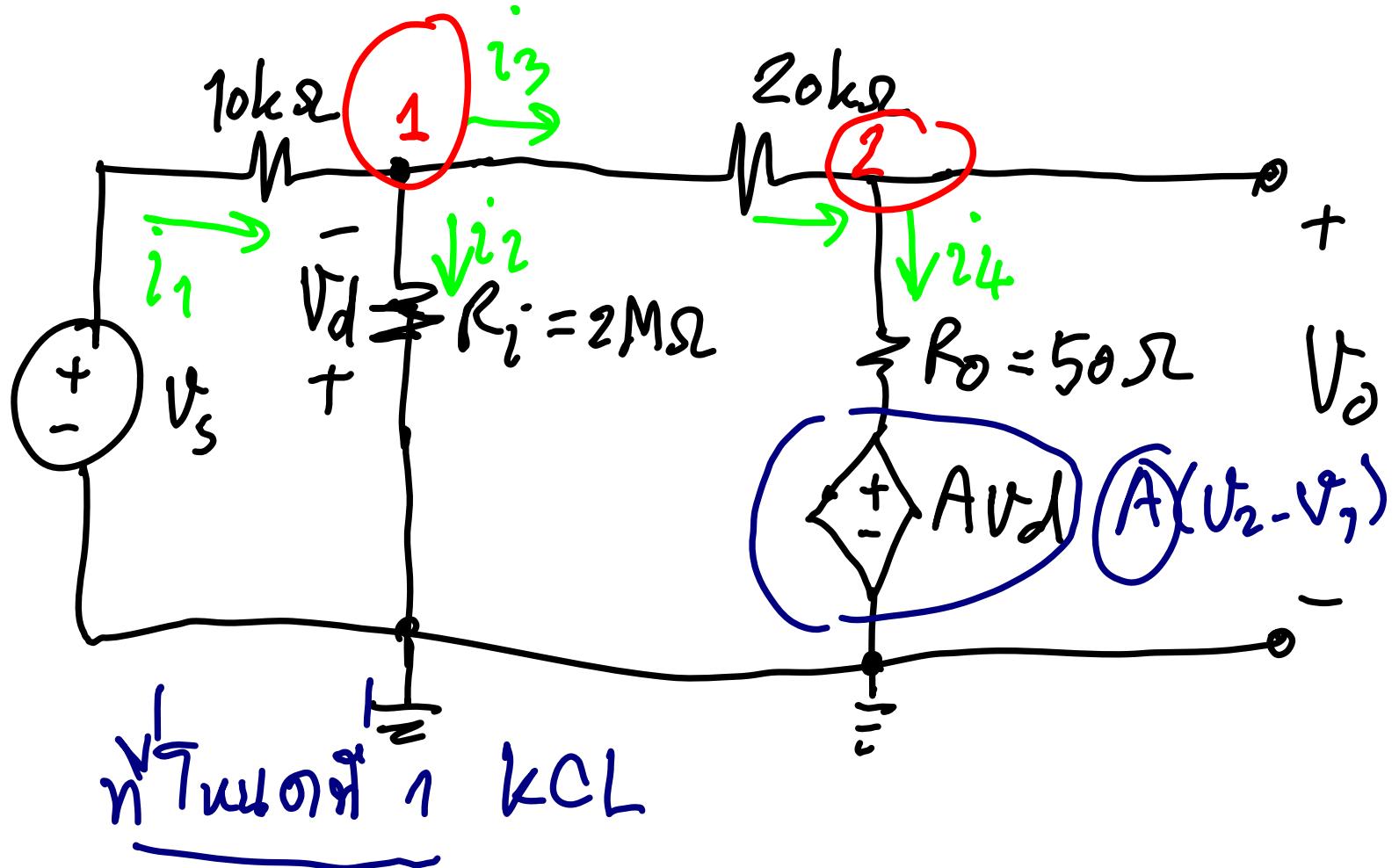

$$i_1 = i_2 + i_3 \Rightarrow \frac{V_s - V_1}{10k\Omega} = \frac{V_1}{R_i = 2M\Omega} + \frac{V_1 - V_2}{20k\Omega}$$

$$\text{ອຳນວຍ} \quad 2 \times 10^6 \text{ ນິ້ນລະວົງ}$$

$$200V_s - 200V_1 = V_1 + 100V_1 - 100V_2$$

$$200V_s = 301V_1 - 100V_2$$

$$V_1 = \frac{200V_s + 100V_2}{301 \approx 300} = \frac{2V_s + V_2}{3} \times$$

ກຳນົດວ່າ

$$\frac{V_1 - V_2}{20k\omega} = \frac{V_2 - Avd}{50}$$

$$Vd = -V_1$$

$$\text{PNA } A = 2 \times 10^5 \text{ for } V_d = -V_1$$

$$\frac{V_1 - V_2}{20 \text{ k}\Omega} = \frac{V_2 + 2 \times 10^5 V_1}{50}$$




$$\text{Now } V_1 = \frac{2}{3} V_S + \frac{V_2}{3}$$

$$-53.33 \times 10^6 V_S = 26.66 \times 10^6 V_2 \rightarrow V_0$$

$$\boxed{\frac{V_2}{V_S} = -2}$$

$\Rightarrow$  close loop gain

# Inverting Amplifier

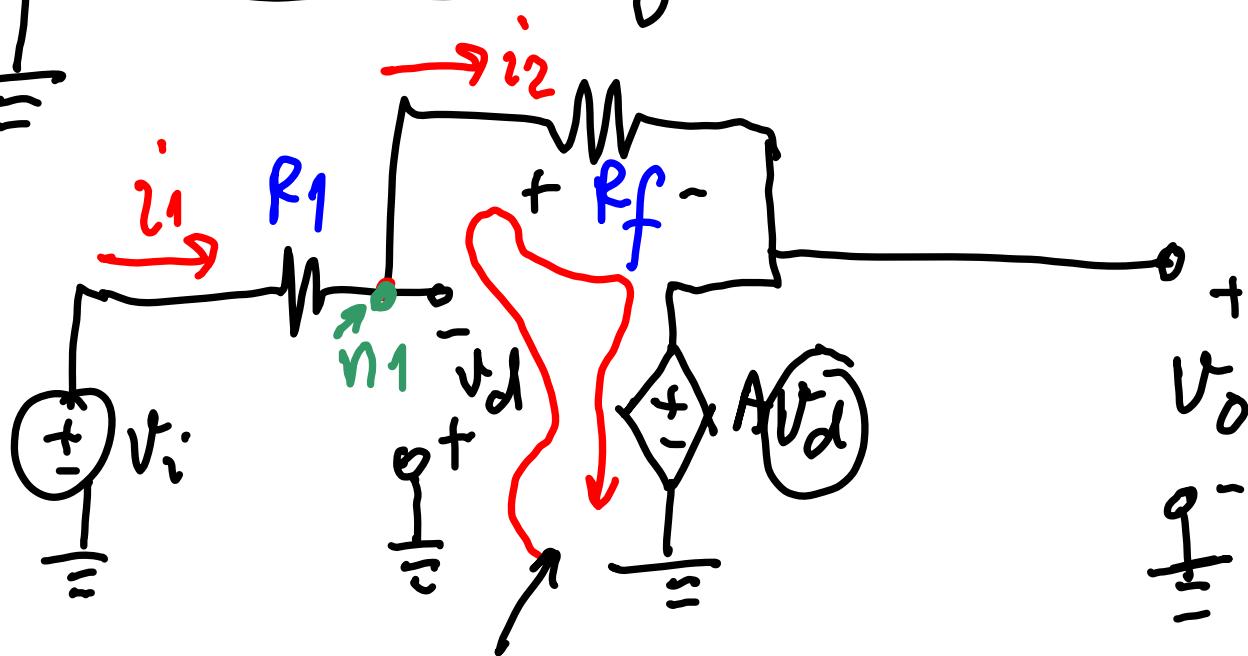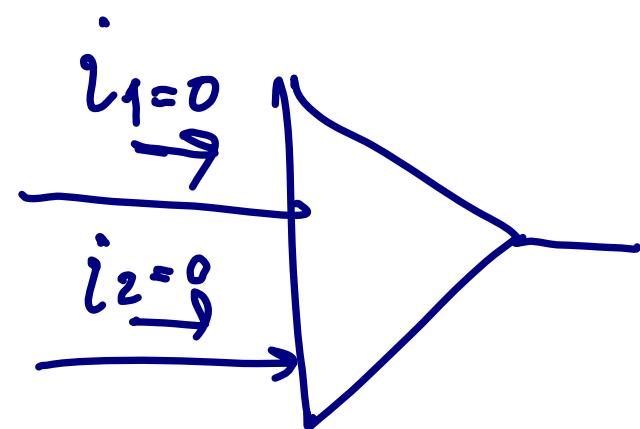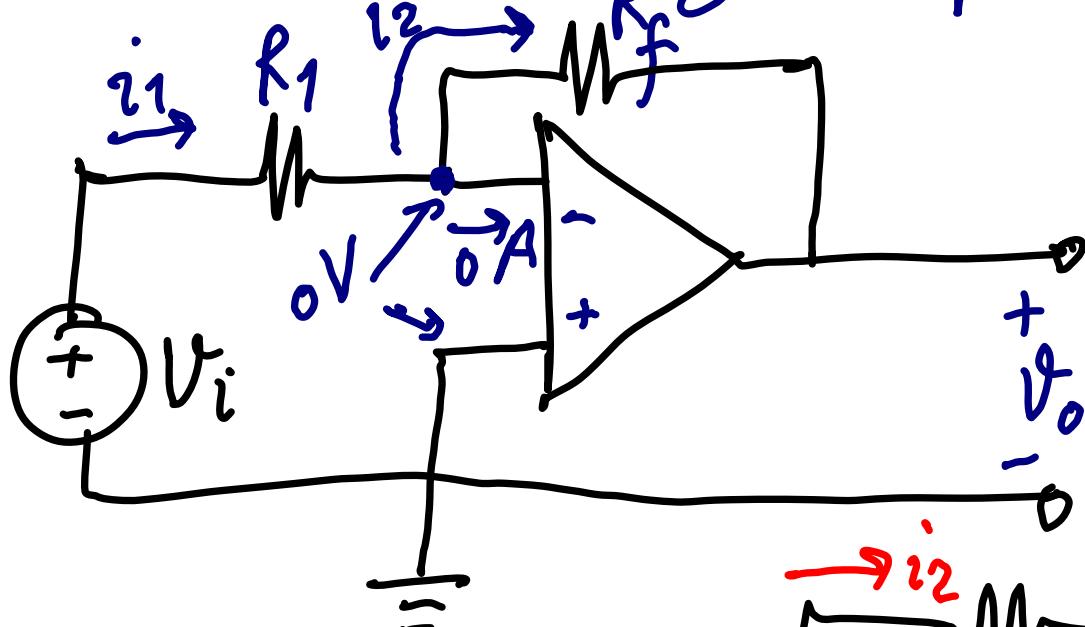

የኝርድ KCL ከተደረገ ነት ማጠናል.

$$\frac{V_i + V_d}{R_1} = -\frac{V_d - V_o}{R_f} \quad \text{--- } ①$$

በዚህም  $V_d = 0$

$$\frac{V_i}{R_1} = -\frac{V_o}{R_f}$$
$$\frac{V_o}{V_i} = -\frac{R_f}{R_1}$$

\* \* \* \* \*

112Bn<sup>1</sup> 2 (inverting)

$$\frac{V_i + V_d}{R_1} = -\frac{V_d - V_o}{R_f} \quad \text{--- } ②$$

$$i_2 = \frac{-V_d - V_o}{R_f} \quad \text{--- } ③$$

$$③ \rightarrow ② \Rightarrow \frac{V_i + V_d}{R_1} = i_2 \quad \text{--- } ④$$

Now KVL  $V_o = V_d + i_2 R_f$

$$+ V_d + i_2 R_f + A V_d = 0 \quad \text{--- } ⑤$$

在 ④ 里写入 ⑤

$$V_d + \frac{V_i + V_d}{R_1} \times R_f + A V_d = 0 \quad \text{--- } 6$$

且  $A V_d = V_o$

$$V_d = \frac{V_o}{A} \quad \text{--- } 7$$

在 ⑦ 里写入 ⑥

$$\frac{V_o}{A} + \left( \frac{V_i}{R_1} + \frac{V_o}{A R_1} \right) R_f + A \frac{V_o}{A} = 0 \quad \text{--- } 8$$

$$\frac{V_o}{A} + \frac{V_i R_f}{R_1} + \frac{V_o R_f}{A R_1} + V_o = 0 \quad \text{--- } 9$$


$$V_o \left( 1 + \frac{1}{A} + \frac{R_f}{A R_1} \right) = - V_i \frac{R_f}{R_1}$$

$$\frac{V_o}{V_i} = \frac{-R_f/R_1}{\left( 1 + \frac{1}{A} + \frac{R_f}{A R_1} \right)}$$

$\therefore$   $A > \infty$

$\boxed{\frac{V_o}{V_i} = -\frac{R_f}{R_1}}$

# Non-inverting Amplifier

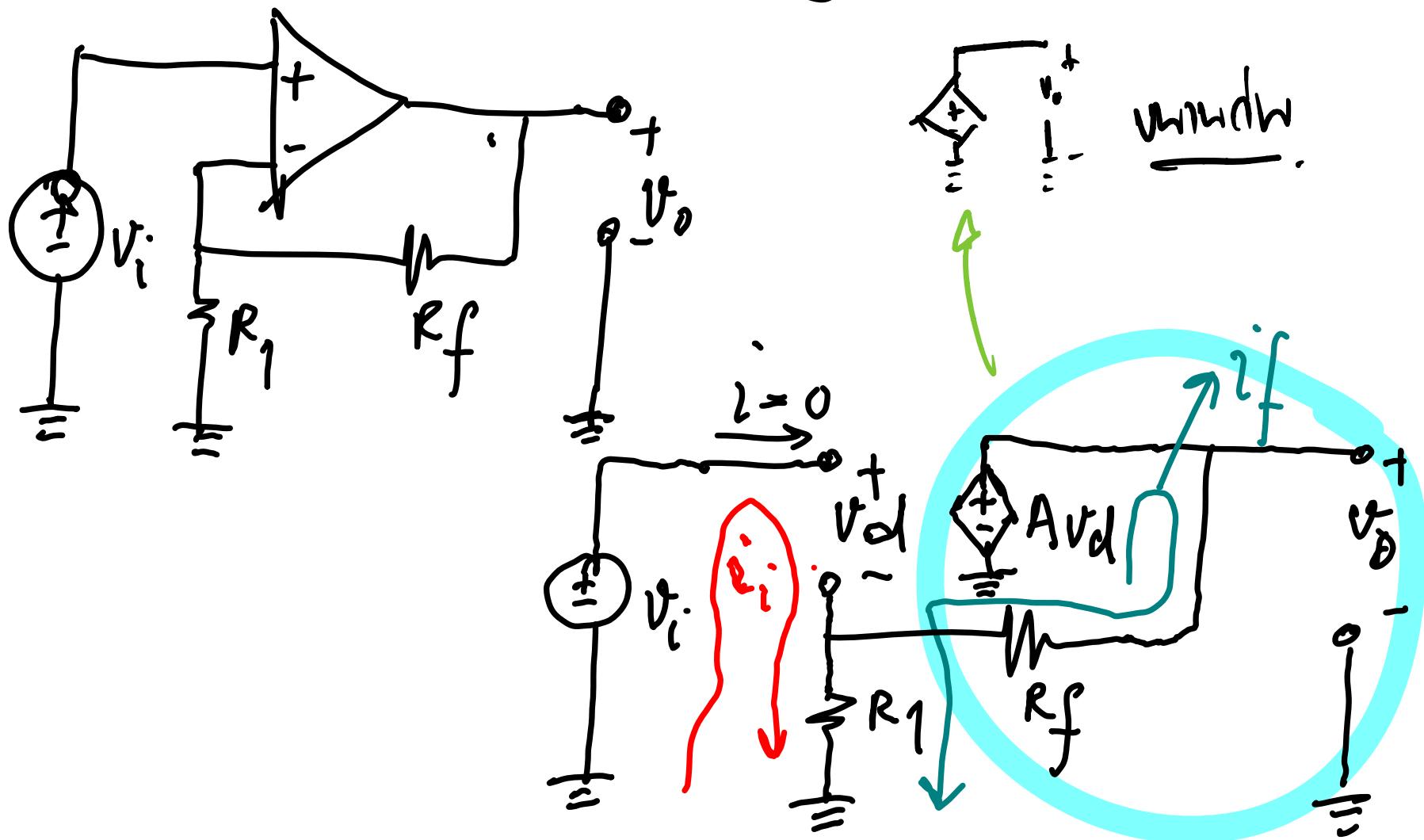

ဓានុរ័យ KVL នៃ loop (ii) ដើម្បី

$$-V_i + V_d + i_f R_1 + i_f R_1 = 0 \quad \text{--- (1)}$$

$$i_i = 0 \quad \xrightarrow{\text{Law (1)}} i_1 = 0$$

នៃ loop (if)  $V_0 = V_{ad}$  ក្នុងលទ្ធផល -

$$-V_0 + i_f R_f + i_f R_1 + i_f R_1 = 0 \quad \text{--- (2)}$$

$$V_0 = i_f (R_f + R_1) \quad \text{--- (3)}$$

នៅ (1)  $i_f = \frac{V_i - V_d}{R_1} \quad \text{--- (4)}$

47 ④ 72 nun zu ③

$$V_0 = \left( \frac{V_i - V_d}{R_1} \right) (R_f + R_1)$$

$$V_0 = \frac{V_i (R_f + R_1)}{R_1} - \frac{V_d (R_f + R_1)}{R_1}$$


Rechnen  $V_d = \frac{V_0}{A}$

$$V_0 = \frac{V_i (R_f + R_1)}{R_1} - \frac{V_0}{A} \frac{(R_f + R_1)}{R_1}$$


$$V_o \left( 1 + \frac{R_f + R_1}{AR_1} \right) = V_i \cdot \frac{(R_f + R_1)}{R_1}$$

DAC  
Digital Analog Converter
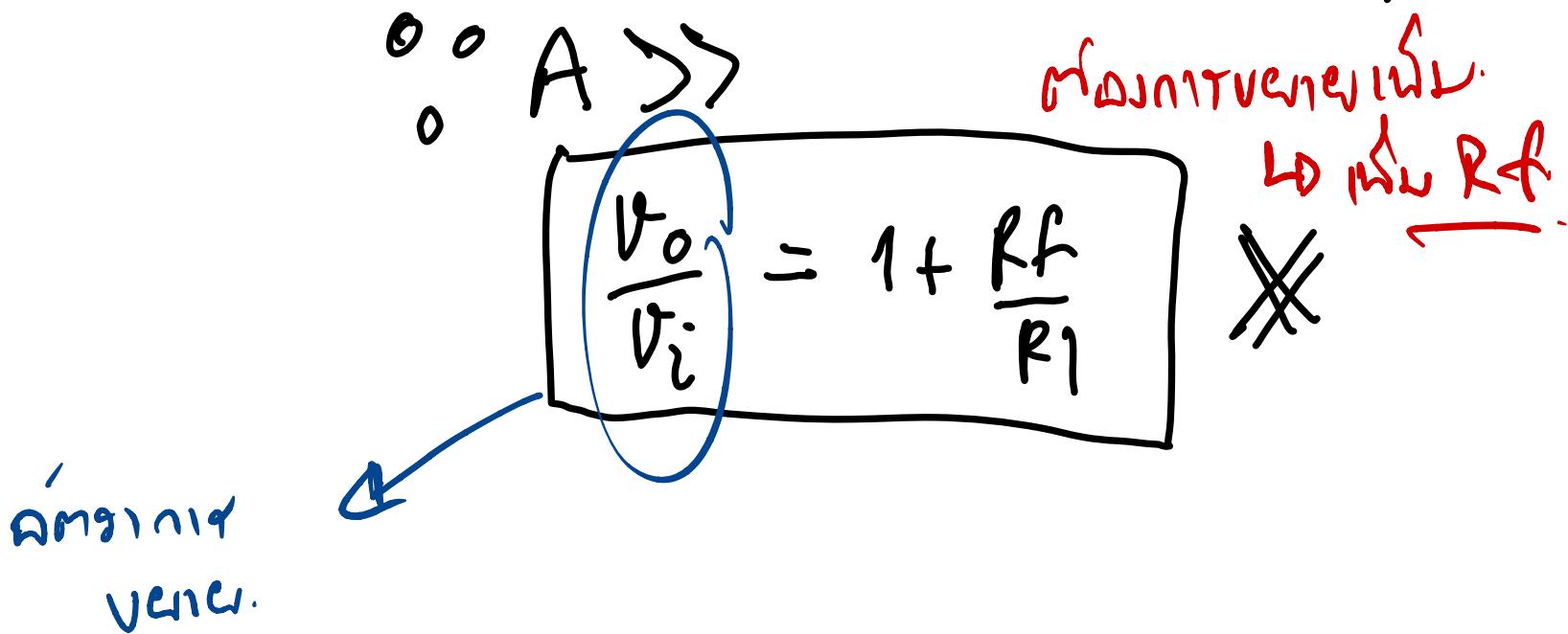
$$\frac{V_o}{V_i} = \frac{(R_f + R_1)}{R_1} \cdot \frac{1}{\left( 1 + \frac{R_f + R_1}{AR_1} \right)}$$



# Inverting Summing Amplifier

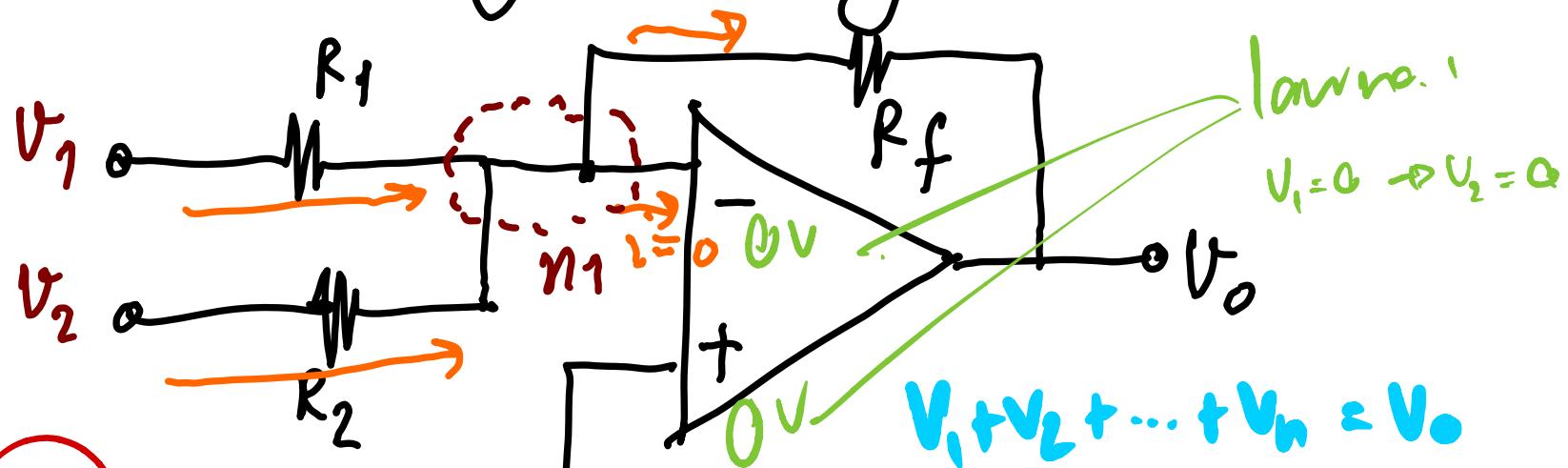

node analysis


at node  $n_1$  ( $k \ll L$ ) ( $V_d \approx 0$ )


$$\frac{V_1 - 0}{R_1} + \frac{V_2 - 0}{R_2} = \frac{0 - V_o}{R_f}$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = -\frac{V_o}{R_f} \Rightarrow V_o = -\left(\frac{V_1 R_f}{R_1} + \frac{V_2 R_f}{R_2}\right)$$

inverting  $\rightarrow V_o = -(V_1 + \dots + V_n)$

# Subtracting Amplifier

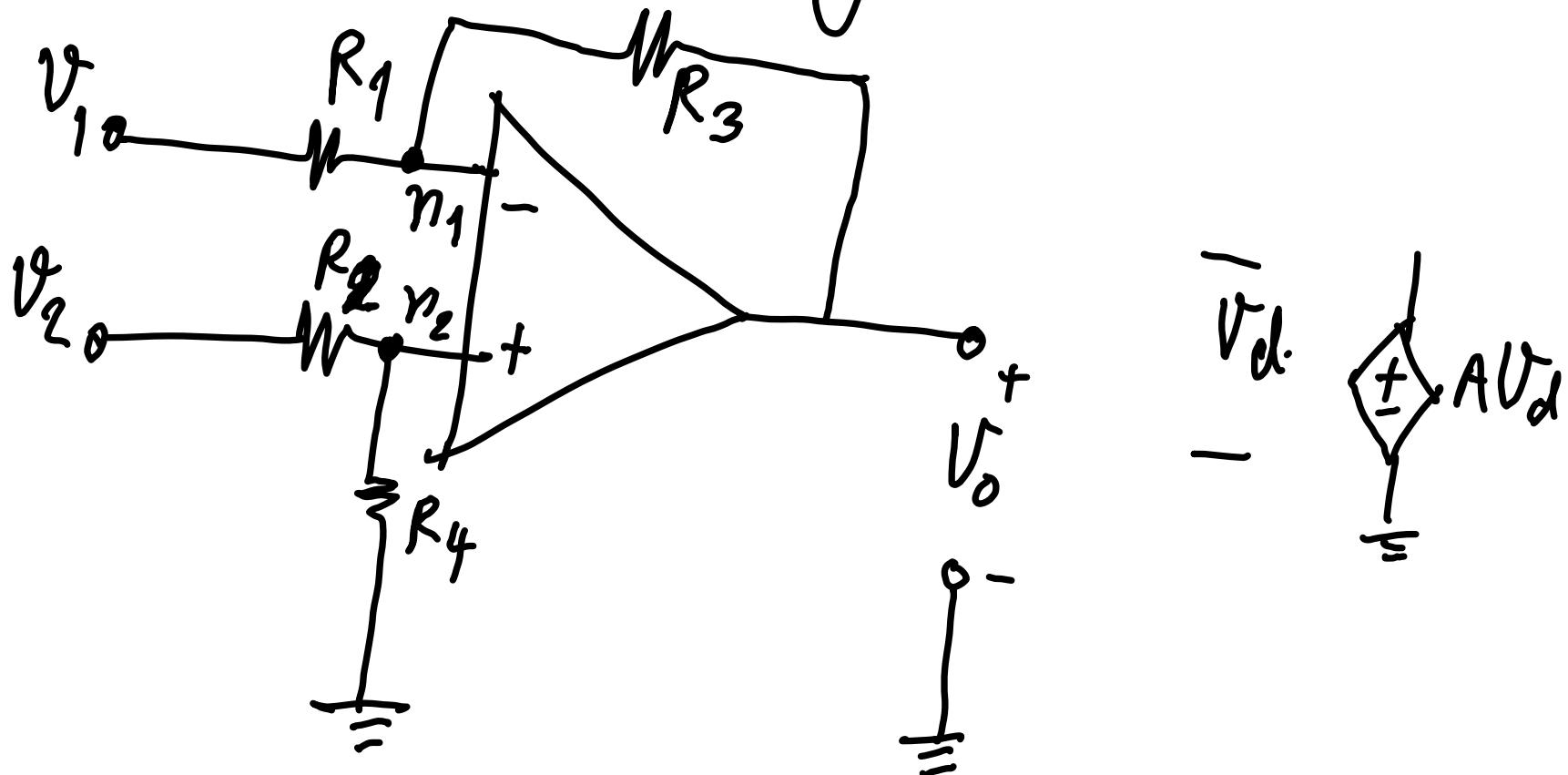

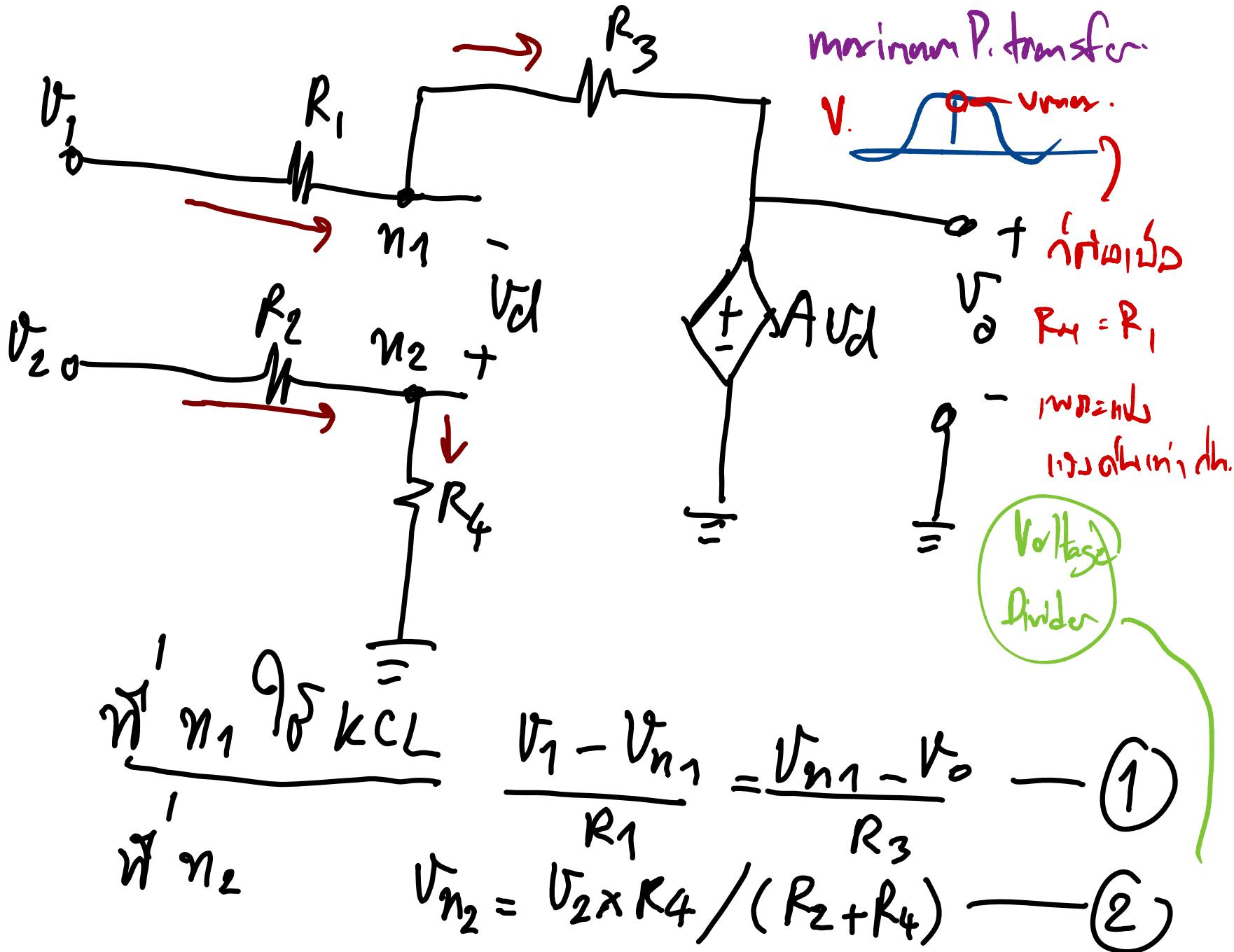

$$\text{According to } V_{n_1} = V_{n_2} \text{ from } ① \text{ Law no. 2 } V_1 = V_2 \\ \therefore V_{n_1} = V_{n_2}$$

$$\frac{V_1}{R_1} - V_{n_1} \left( \frac{1}{R_1} + \frac{1}{R_3} \right) + \frac{V_0}{R_3} = 0 \quad \text{--- } ③$$

$$\text{Now } V_{n_1} \text{ is } V_{n_2} = \frac{V_2 \cdot R_4}{R_2 + R_4}$$

$$\frac{V_1}{R_1} - \left( \frac{V_2 \cdot R_4}{R_2 + R_4} \right) \left( \frac{1}{R_1} + \frac{1}{R_3} \right) + \frac{V_0}{R_3} = 0 \quad \text{--- } ④$$

$$\frac{V_1}{R_1} - V_2 \left( \frac{R_4}{R_1(R_2 + R_4)} + \frac{R_4}{R_3(R_2 + R_4)} \right) + \frac{V_0}{R_3} = 0 \quad \text{--- } ⑤$$

$\boxed{\frac{R_3}{R_1} = \frac{R_4}{R_2} = n}$

$$R_3 = n R_1 \text{ if } R_2 = n R_4 \quad \text{--- } ⑥$$

⑥  $\text{from } ⑤.$

$$\frac{V_1}{R_1} - V_2 \left( \frac{nR_2}{R_1(R_2+nR_2)} + \frac{nR_2}{R_3(R_2+nR_2)} \right) + \frac{V_0}{R_3} = 0 \quad (7)$$

$$\frac{V_1}{R_1} - \frac{V_2}{R_1} \left( \frac{n}{(1+n)} \right) \left( \frac{1+n}{n} \right) + \frac{V_0}{R_3} = 0$$

$$\frac{V_1 - V_2}{R_1} + \frac{V_0}{R_3} = 0$$

$$V_0 = (V_2 - V_1) \left( \frac{R_3}{R_1} \right)^n$$


$$\therefore \text{if } n = R_3 = R_1$$

$V_0 = V_2 - V_1$  \*


ANSWER

Cap in DC  
no sig charge

# Differentiator Amplifier

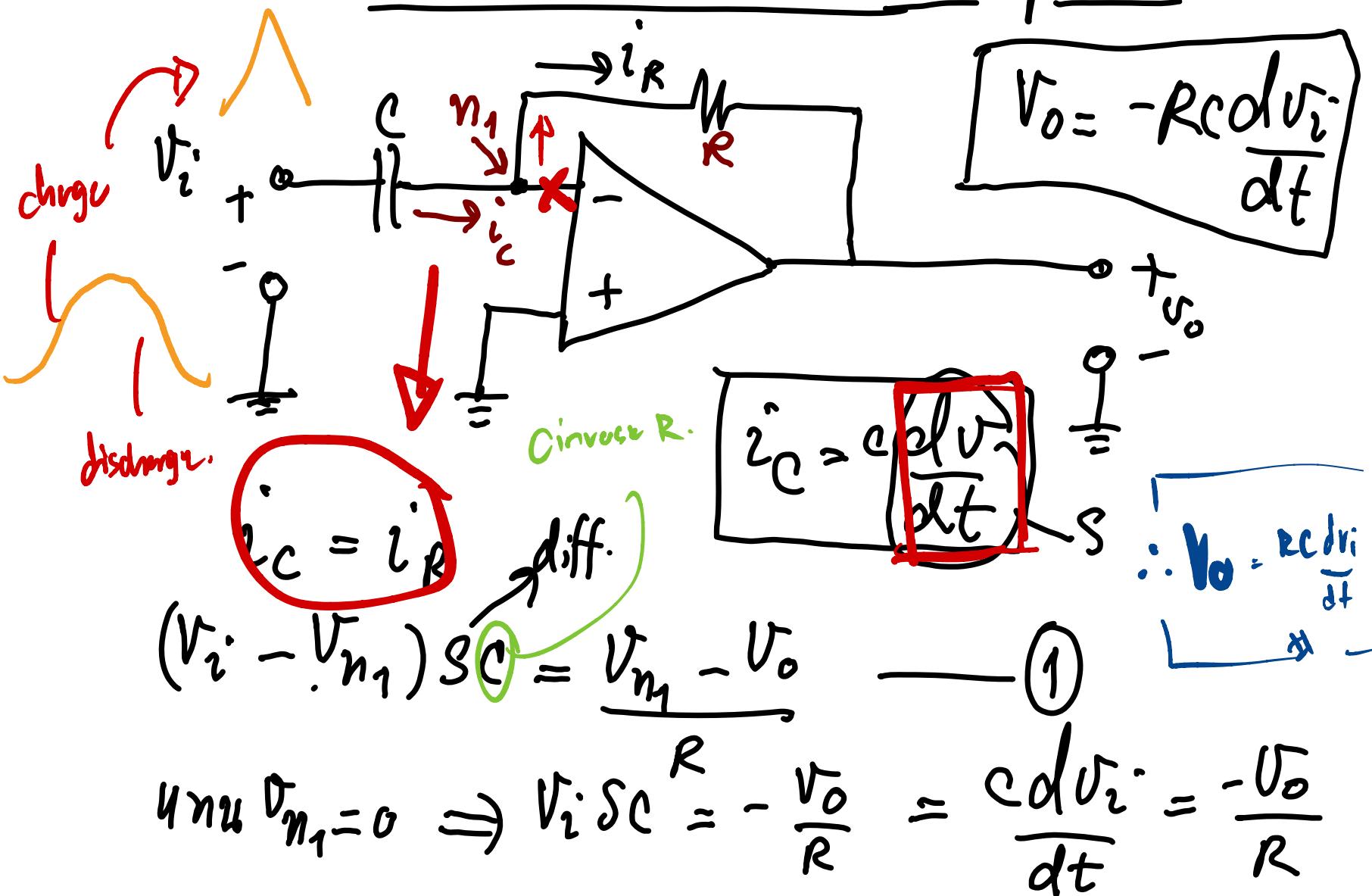

# Integrating Amplifier

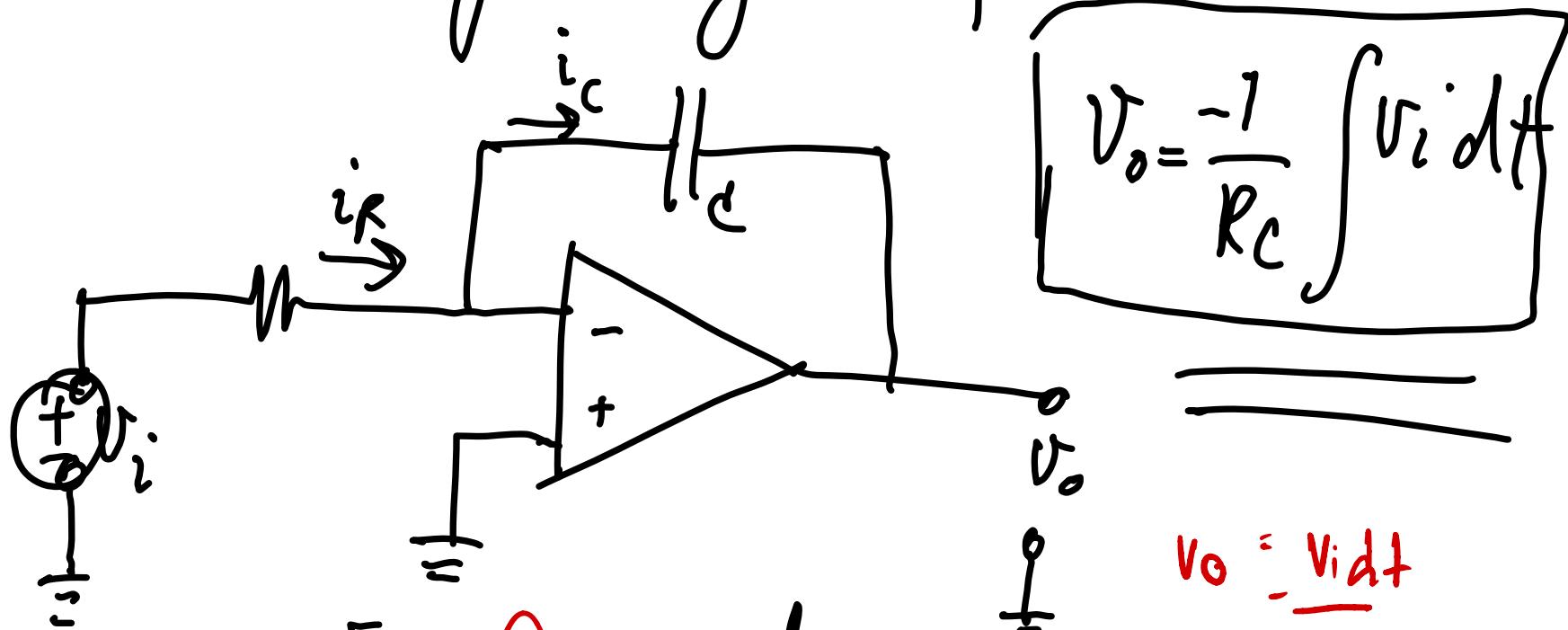

$$V_o = -\frac{1}{R_c} \int V_i dt$$

$$\frac{V_i}{R} = i_R = \cancel{i_{C_c}} = -C_c \frac{dV_o}{dt}$$

$\downarrow = i_R.$

$$V_o = -\frac{V_i dt}{R \times C}$$

A

$$\therefore \frac{V_i}{R} = -\frac{C dV_o}{dt}$$

$\therefore V_o = \frac{\int V_i dt}{-R C}$